

PASSIVE A/B SWITCHER

There is an inherent problem with most A/B Boxes when running separate effects for each channel. Most A/B Boxes do not ground out the channel not being used, resulting in massive hum + hiss when distortion or fuzz pedals are left on. This design eliminates that problem, and has the purest, non buffered, most transparent tone available.




www.MOUSER.com (800)346-6873
 HAMMOND1590B BOX 546-1590B

Yellow LED 604-L53YD
 Red LED 604-L53HD
 LED Holder 606-4304MC

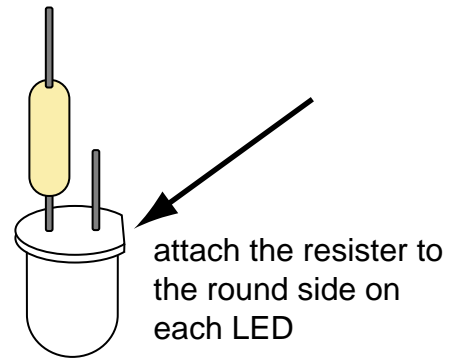
2.1mm DC Jack 163-4302

Switchcraft Mono Jack 502-11
 Switchcraft Stereo Jack 502-12B
 (only for battery powered)

FULLTONE 3PDT SWITCH (available at fulltone.com)



10K 1/4 watt resistor

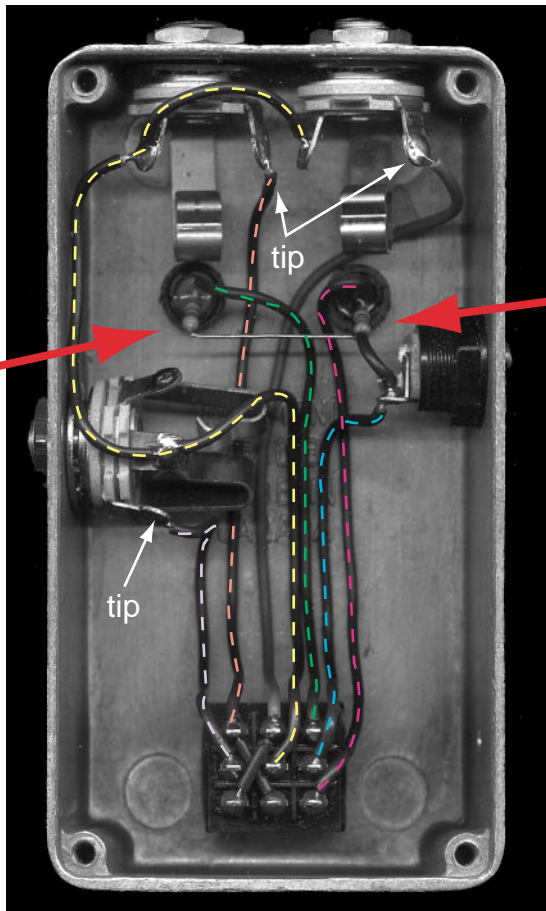

2.2K 1/4 watt resistor

